

Lab 3: Logic Gates

Andrew
Devin
Hyrum
Marcel

Overview



Logic gates



Computer Aided Design (CAD)




Solving real-world problems

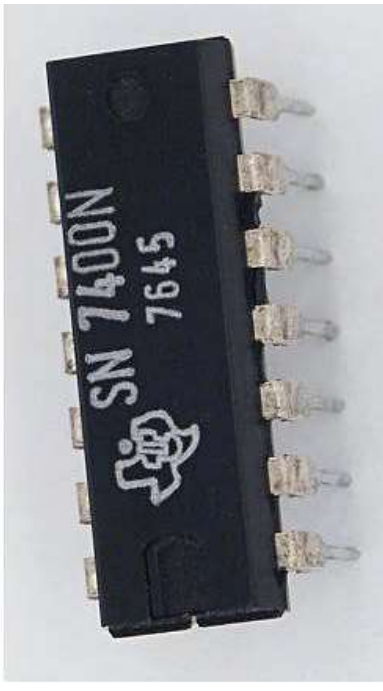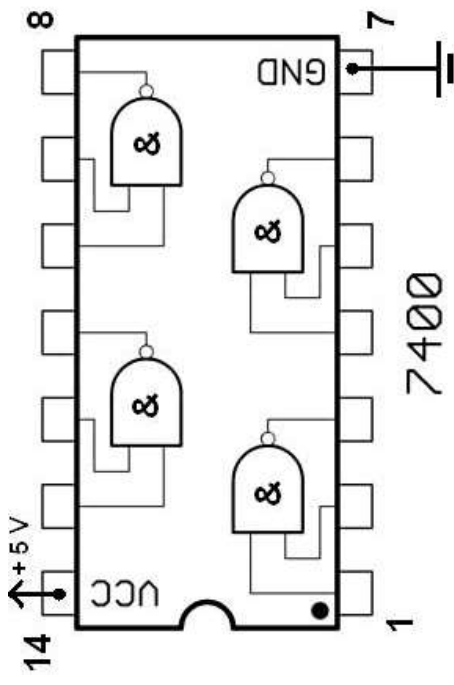

Computer Aided Design (CAD)


$$\text{Alarm} = C'V$$

$$\text{Fan} = TV' + TC$$

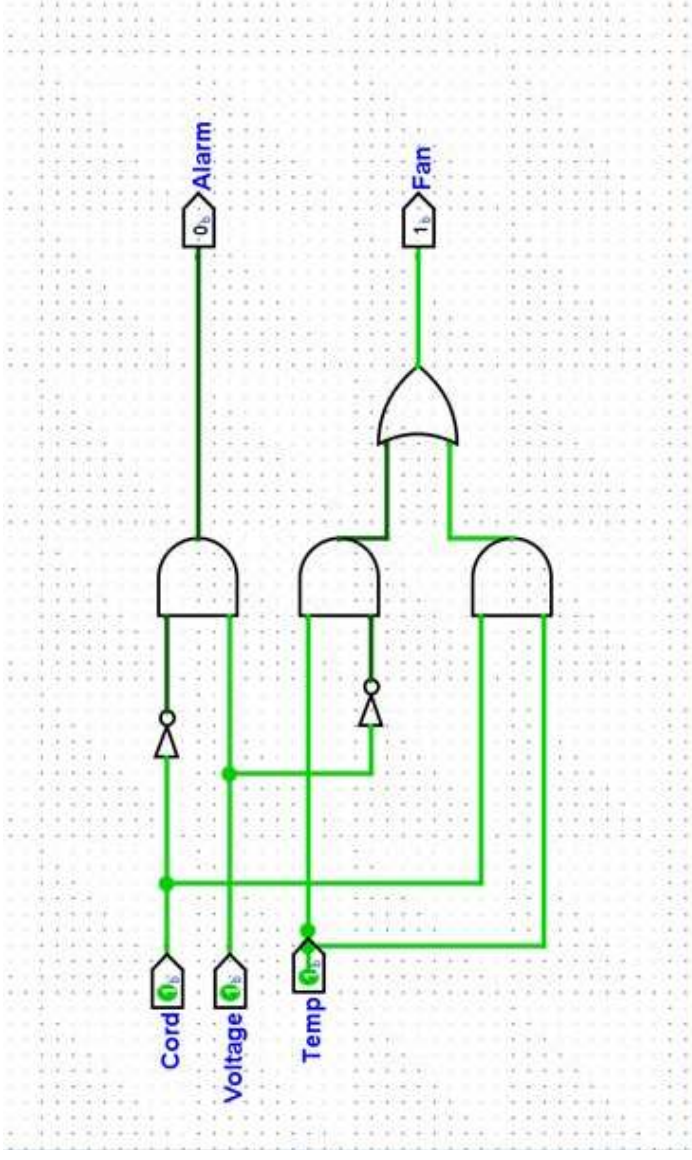

The Circuit

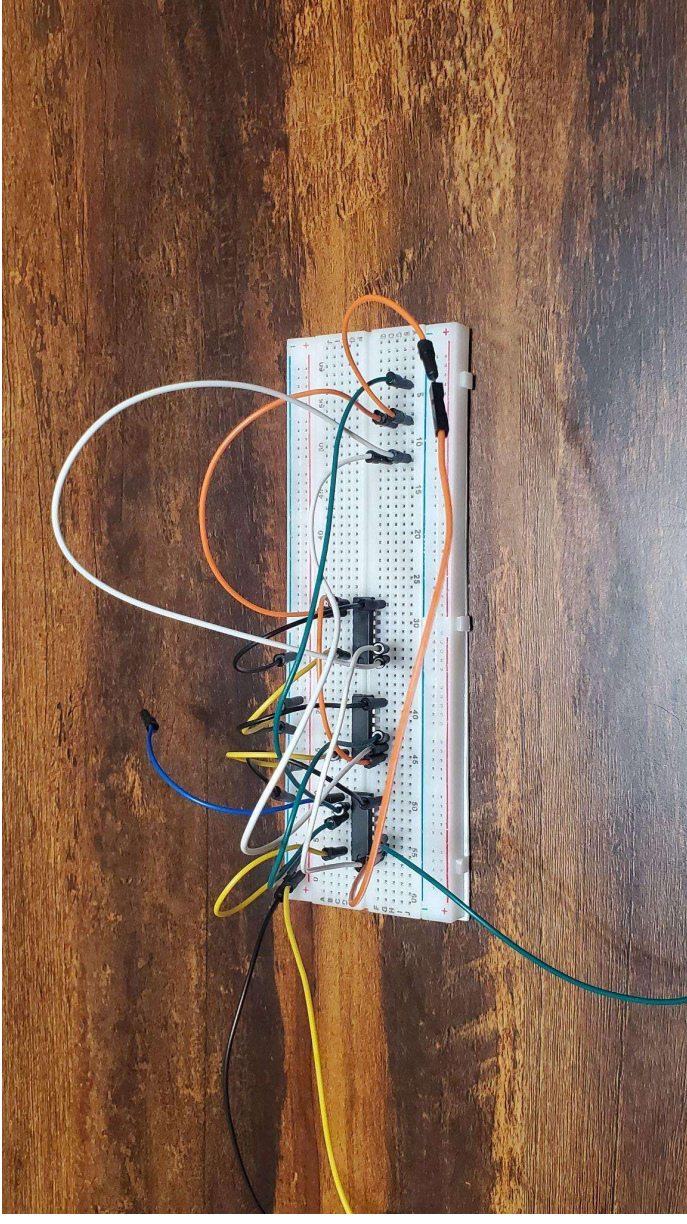- The fan/alarm circuit
 - Using 3 IC's
 - 3 Inputs
 - 2 Outputs
- With the truth table, we tested the circuit to get the outputs



- Legend (Inputs):
 - White: Cord
 - Orange: Voltage
 - Green: Temperature

Conclusion

- Review the basic Logic gates.
- Learn how to use the CAD tool for digital logic simulation.
- Learn how real-world problems may be solved by a simple digital design problem
- Learn how to implement a digital circuit using 74xx family of logic gates.

logisim-evolution/**logisim-evolution**

Digital logic design tool and simulator

